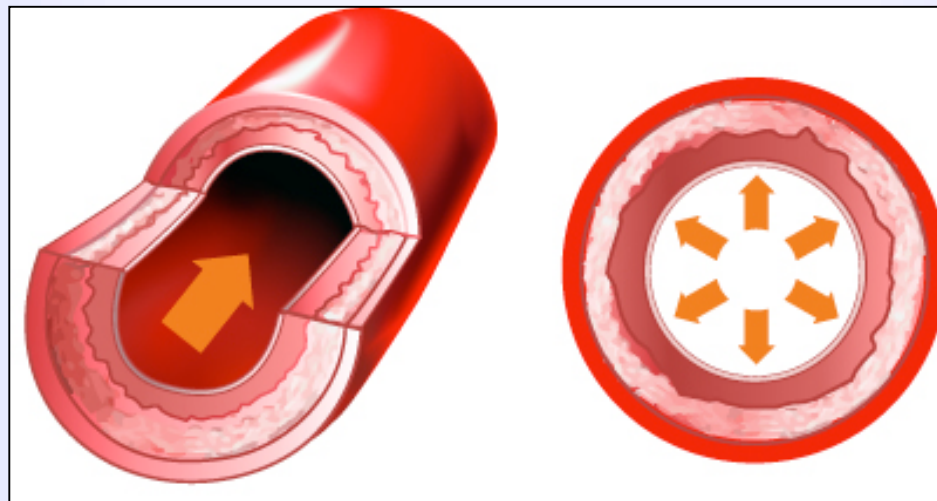


Vascular mechanics modeling





Maxwell Neal


NSR Modeling Course

Aug 29th, 2008


The human cardiovascular system

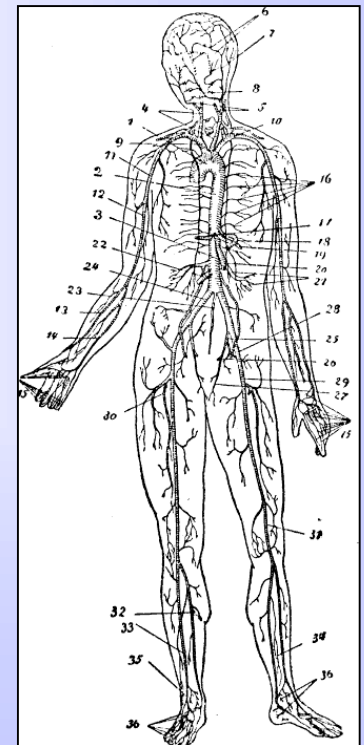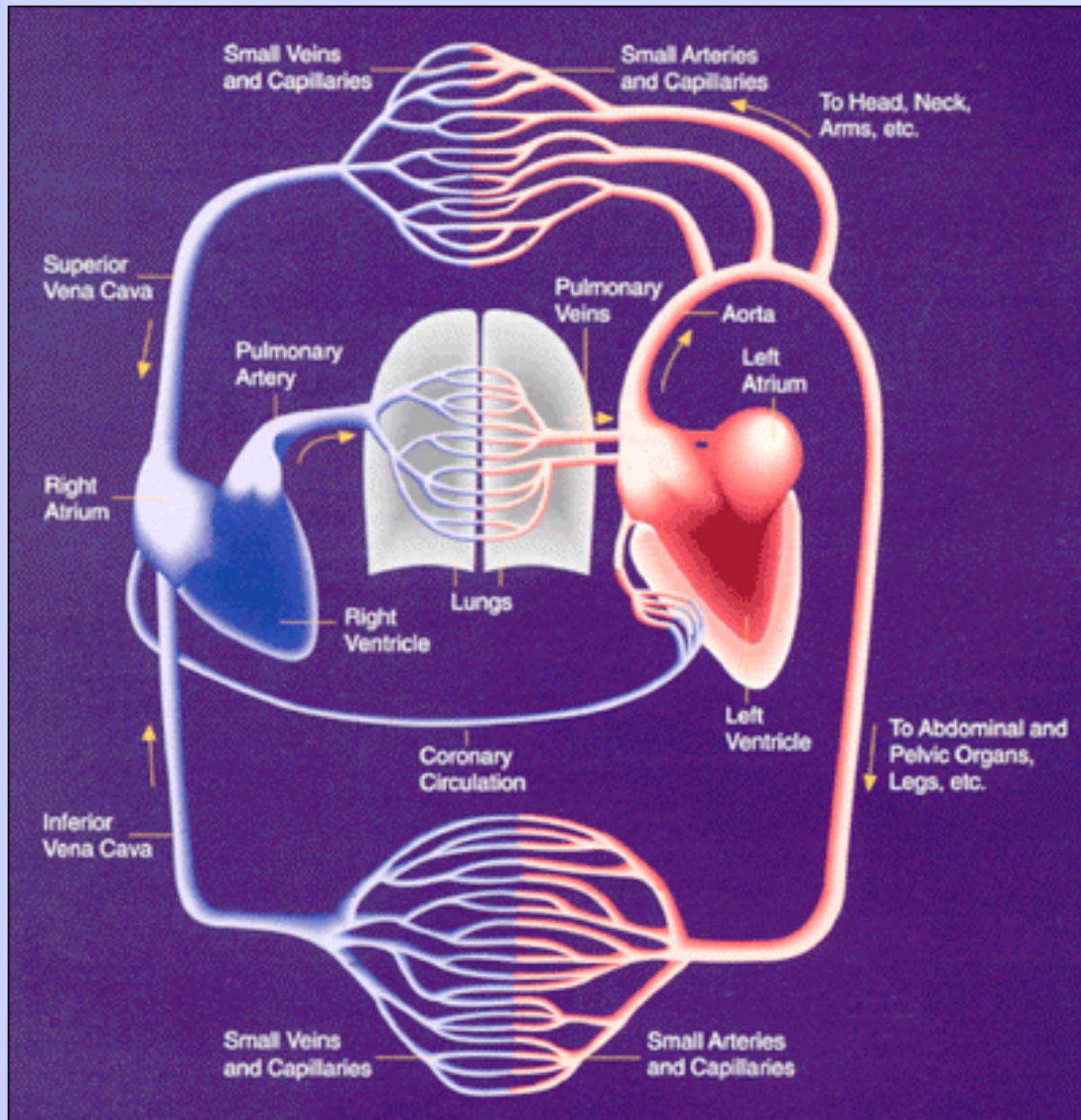

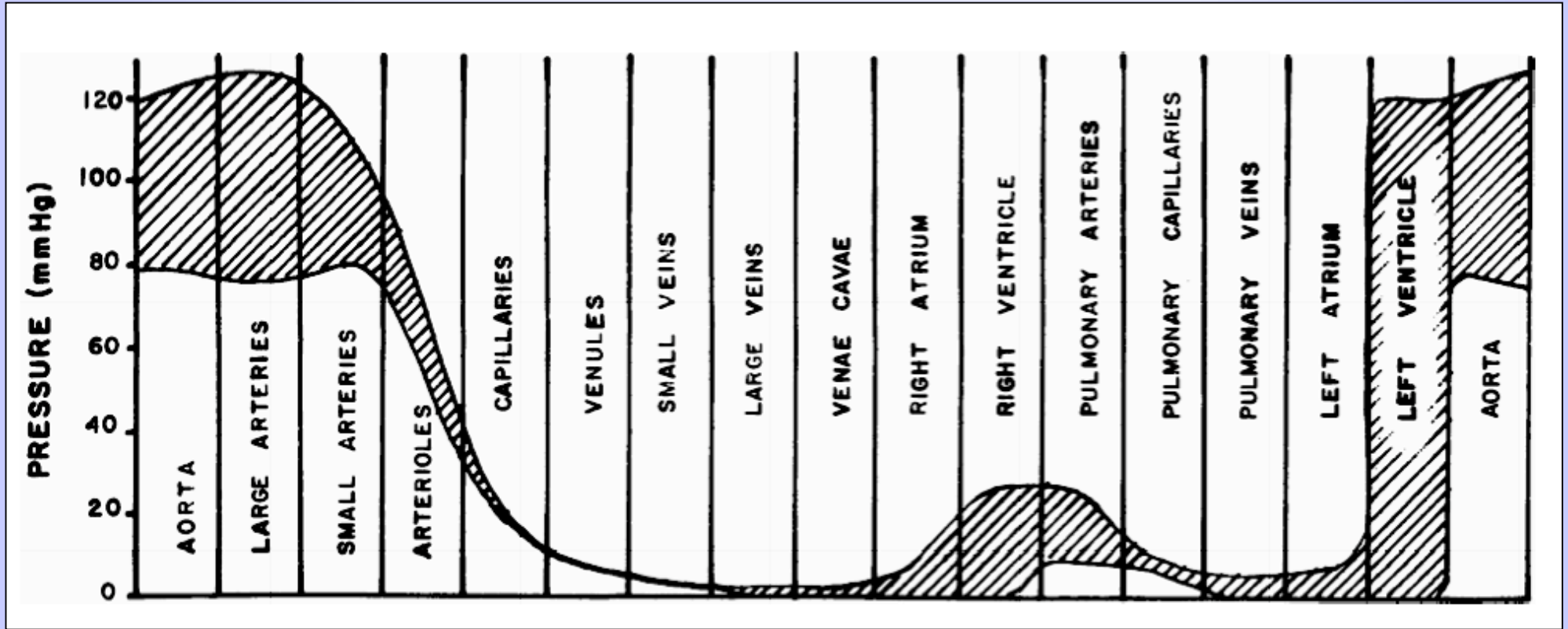Blood pressures in the systemic circulation




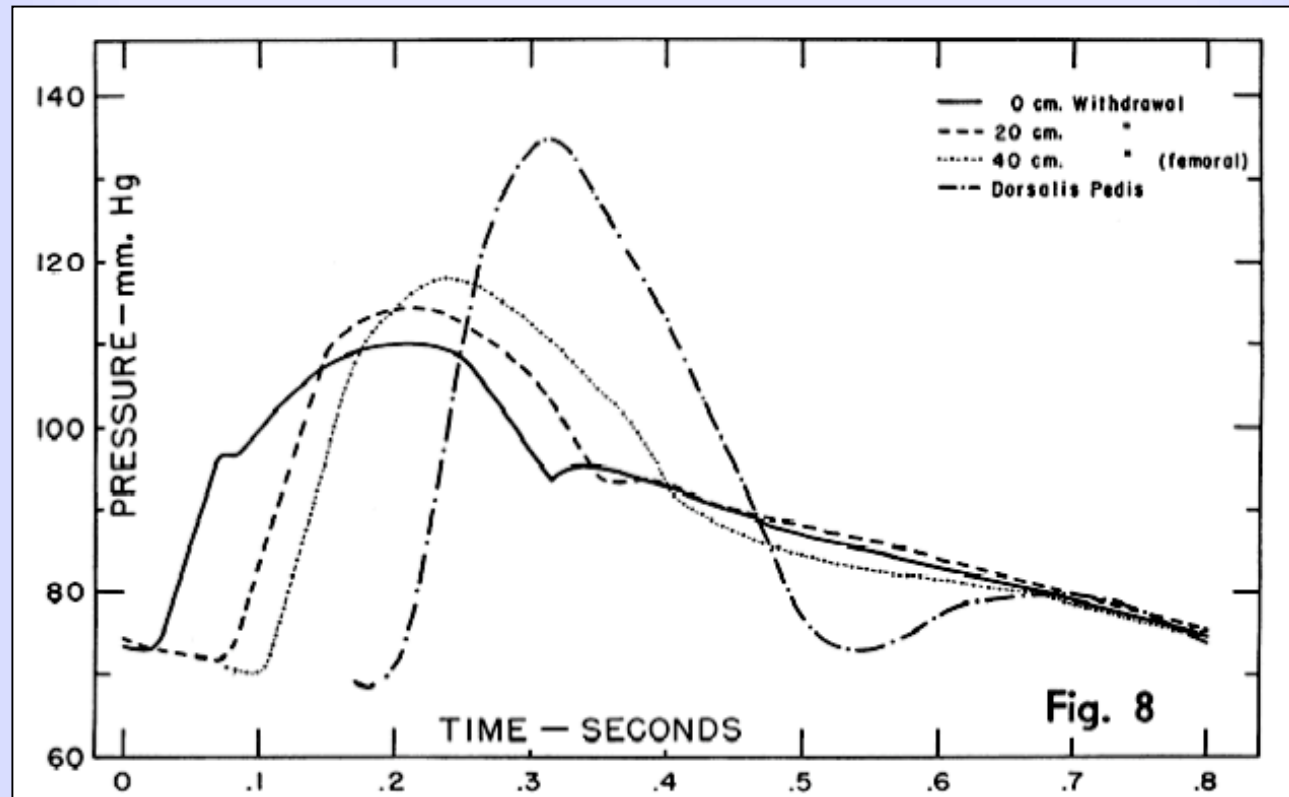Wave reflections in the arterial tree amplify the arterial pulse pressure



From Remington and Wood. *J. Applied Physiology*. 1956


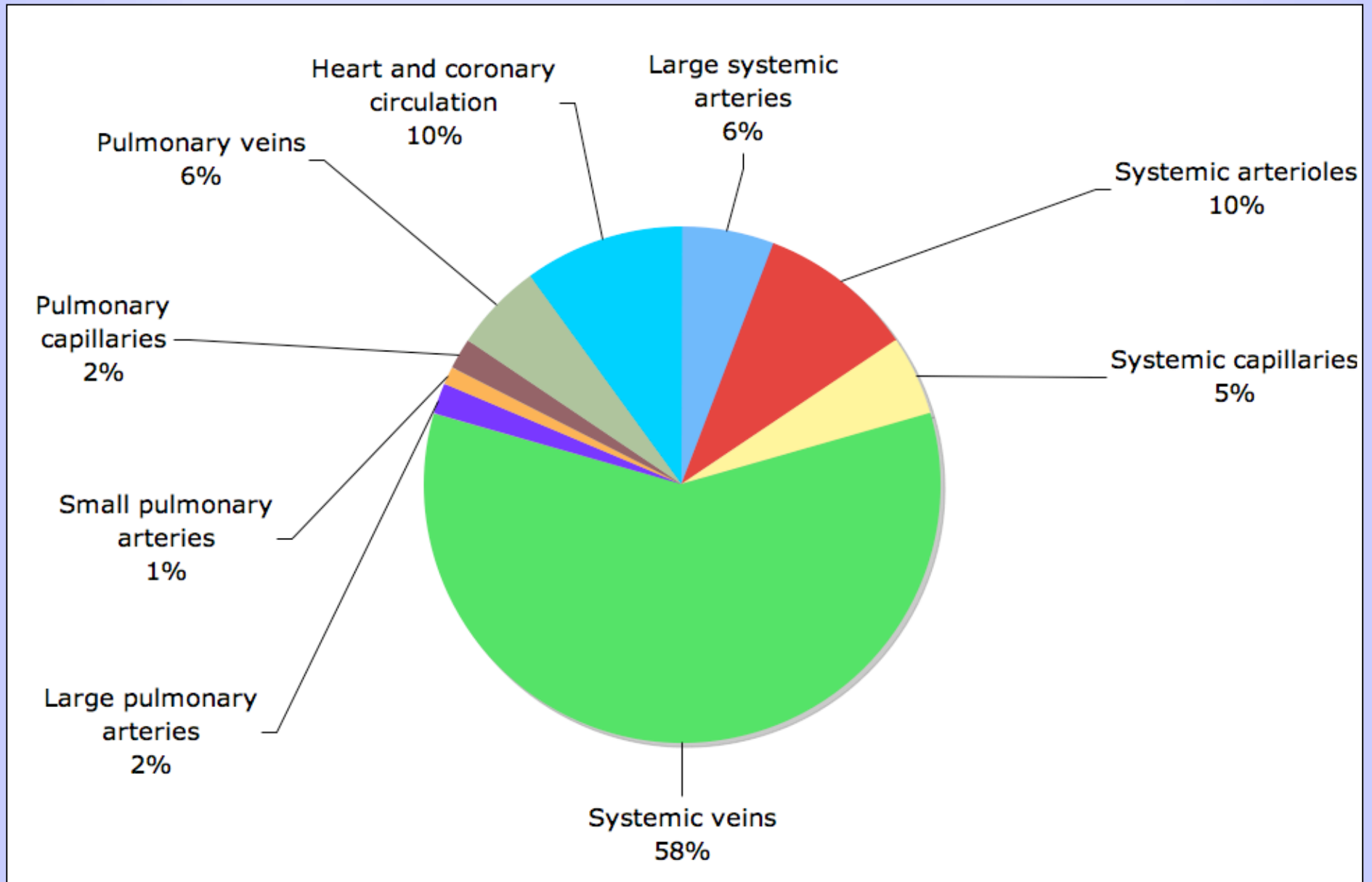
Distribution of blood volumes throughout the circulation




Distribution of blood flows throughout the circulation

<u>Compartment</u>	<u>% of total cardiac output</u>
Coronary circulation	4
Cerebral circulation	12
Peripheral circulation	84
Pulmonary circulation	100

Pressure-volume curves of circulatory vessels are curvilinear but models often use linear approximations

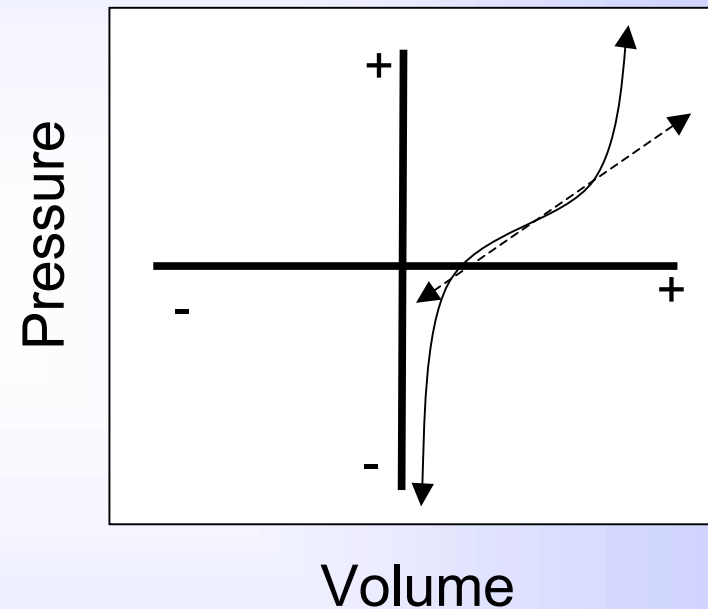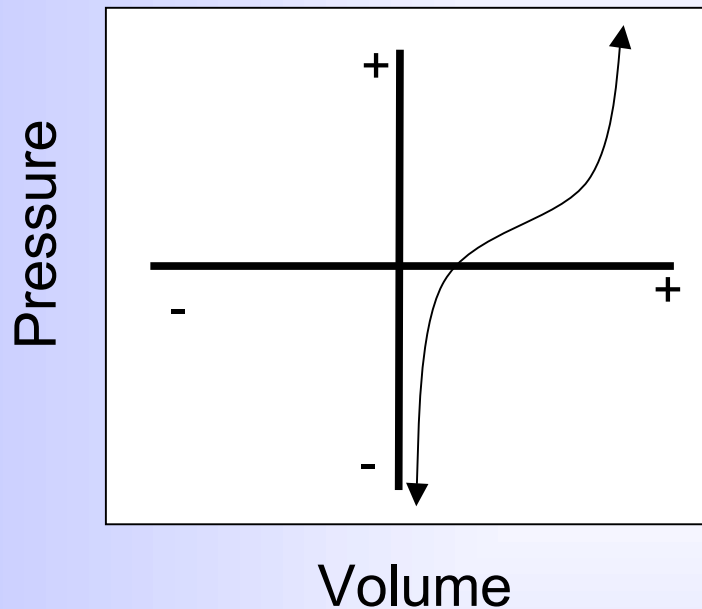

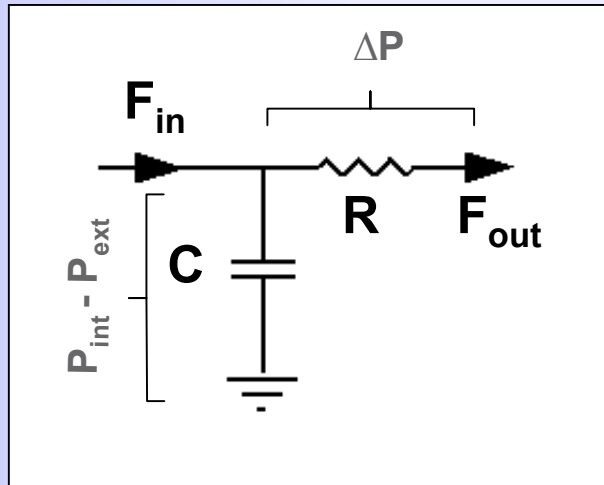The 3-element Windkessel uses circuit laws to simulate a compliant tube



Analogs

Charge : Volume (V)

Voltage : Pressure drop (Pd)

Current : Flow (F)

Capacitance : Compliance (E)

(1/Capacitance = Elastance)

Ohm's Law for fluids

$$F_{out} = \Delta P / R$$


Law of compliance

$$P_{int} - P_{ext} = (V - V_{rest}) / C$$

Kirchoff's Conservation Law

$$dV/dt = F_{in} - F_{out}$$

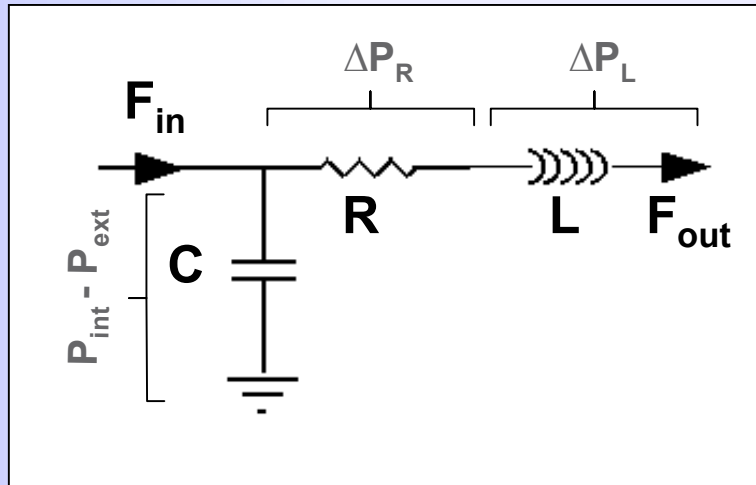The 4-element Windkessel adds fluid momentum



Analogs

Charge : Volume (V)

Voltage : Pressure drop (Pd)

Current : Flow (F)

Capacitance : Compliance (E)

(1/Capacitance = Elastance)

Inductance : Inertance

Ohm's Law for fluids

$$F_{out} = \Delta P_R / R$$

Law of compliance

$$P_{int} - P_{ext} = (V - V_{rest}) / C$$


Law of inertance

$$dF_{out} / dt = \Delta P_L / L$$


Kirchoff's Conservation Law

$$dV / dt = F_{in} - F_{out}$$

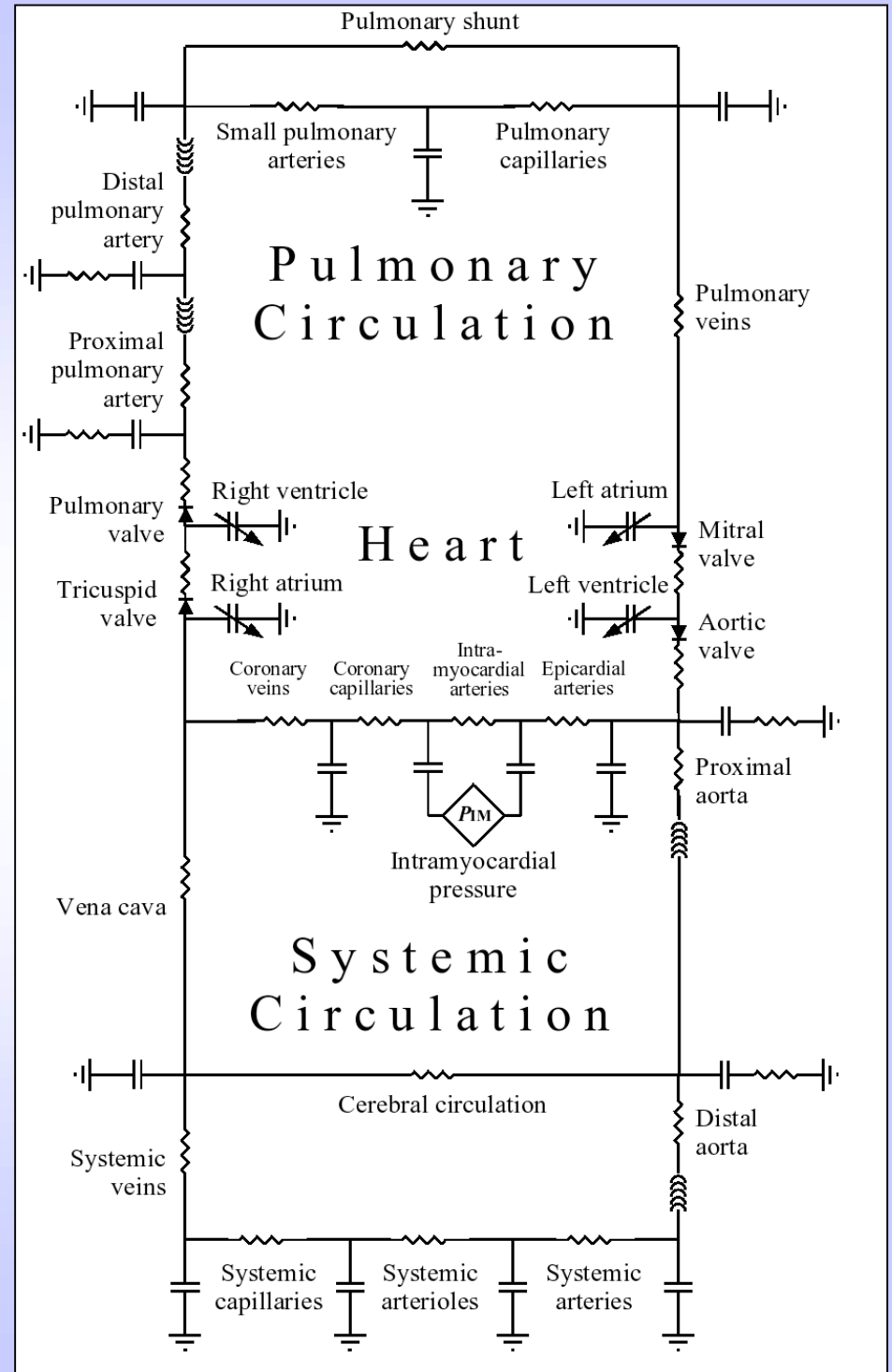
Electrical analog schematic of *spheart.proj*



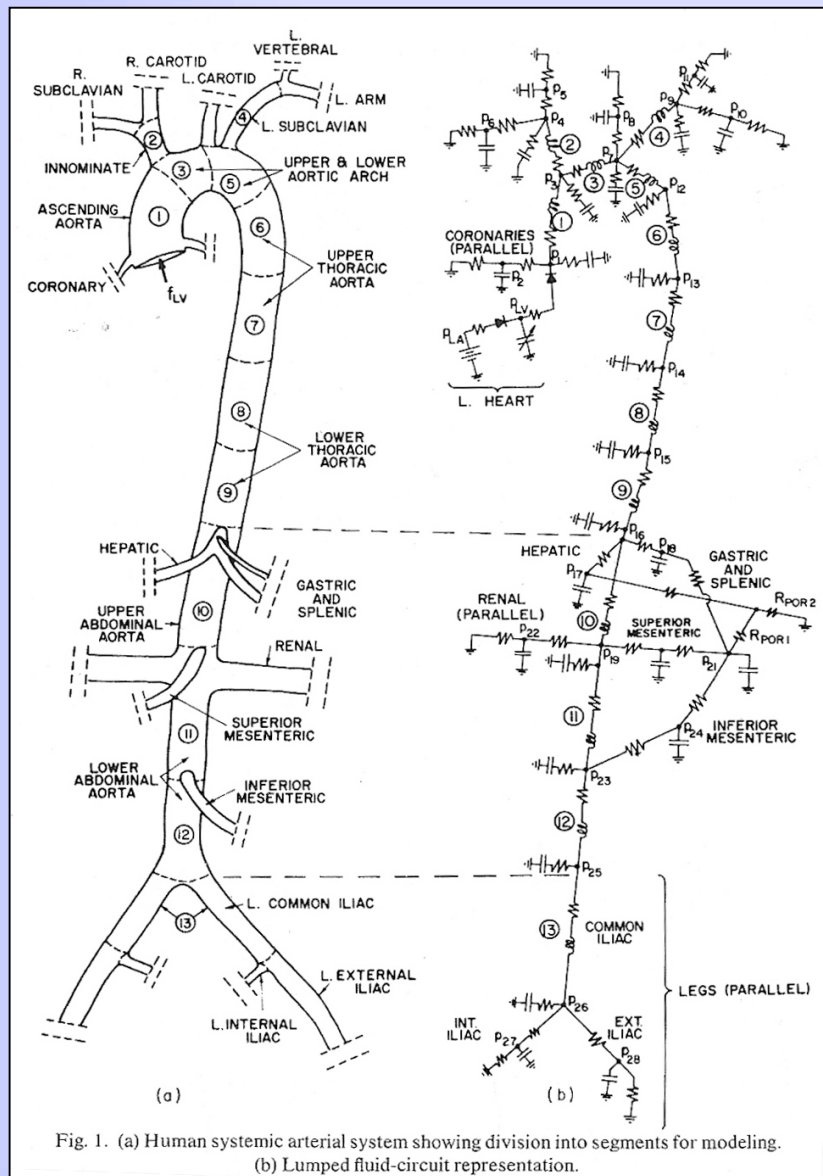
More detailed models of the arterial tree have been used to simulate pulse pressure amplification




Data

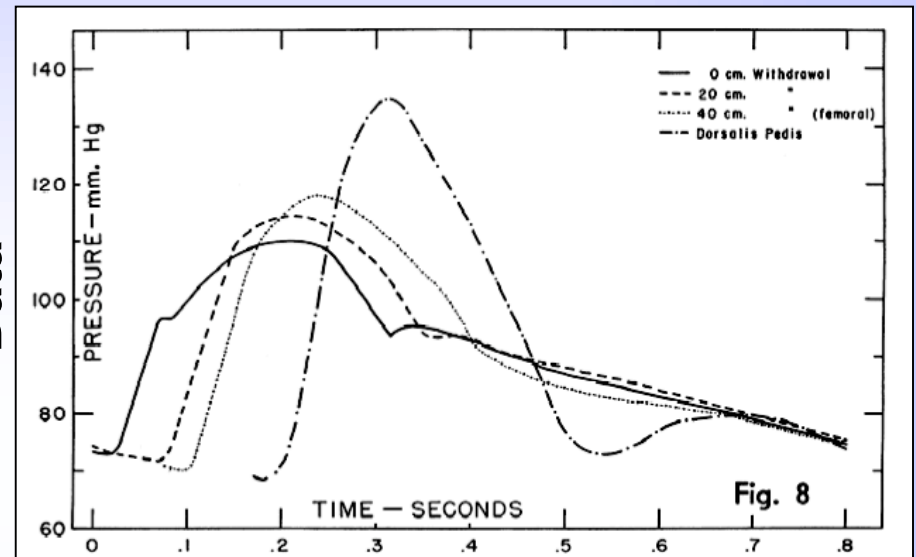

Simulation

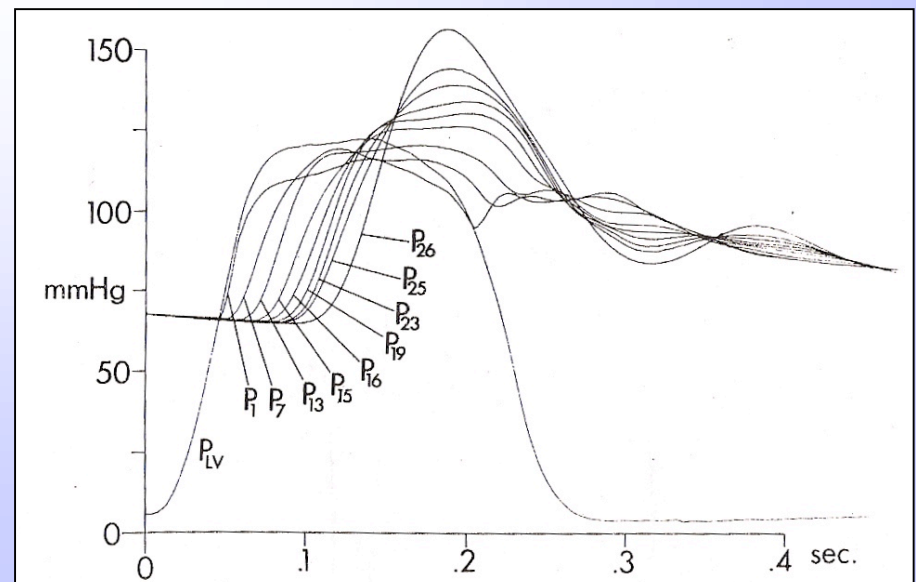

Time to open *spheart_1.proj*

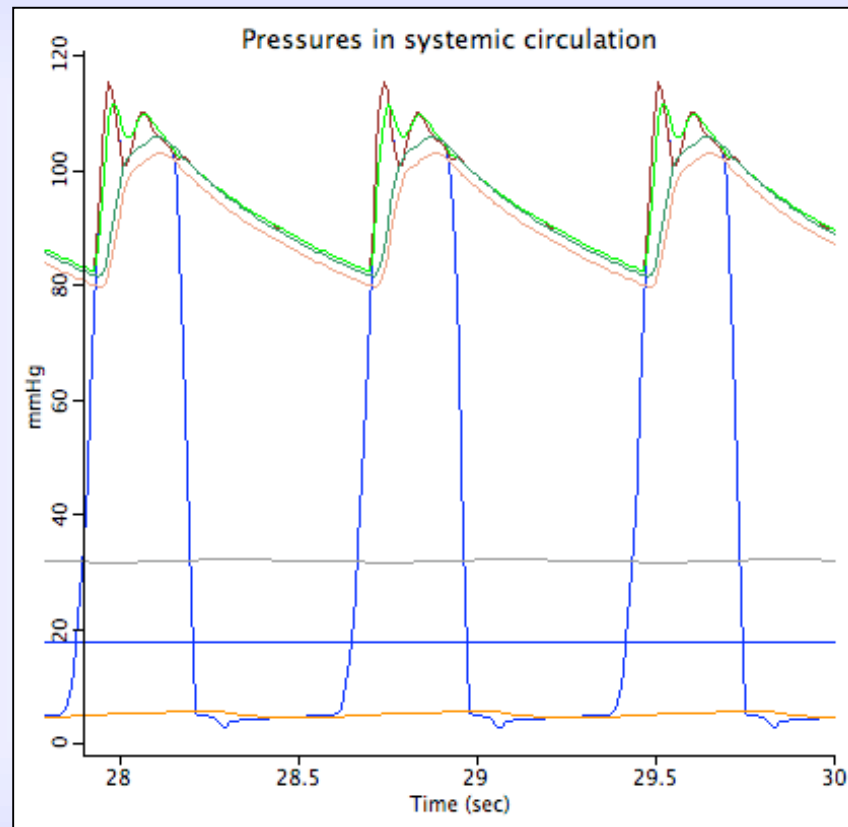


Electrical analog schematic of *spheart_1.proj*

Your mission:

Code a new 3-element Windkessel with volume-dependent resistance for the peripheral systemic capillary segment.

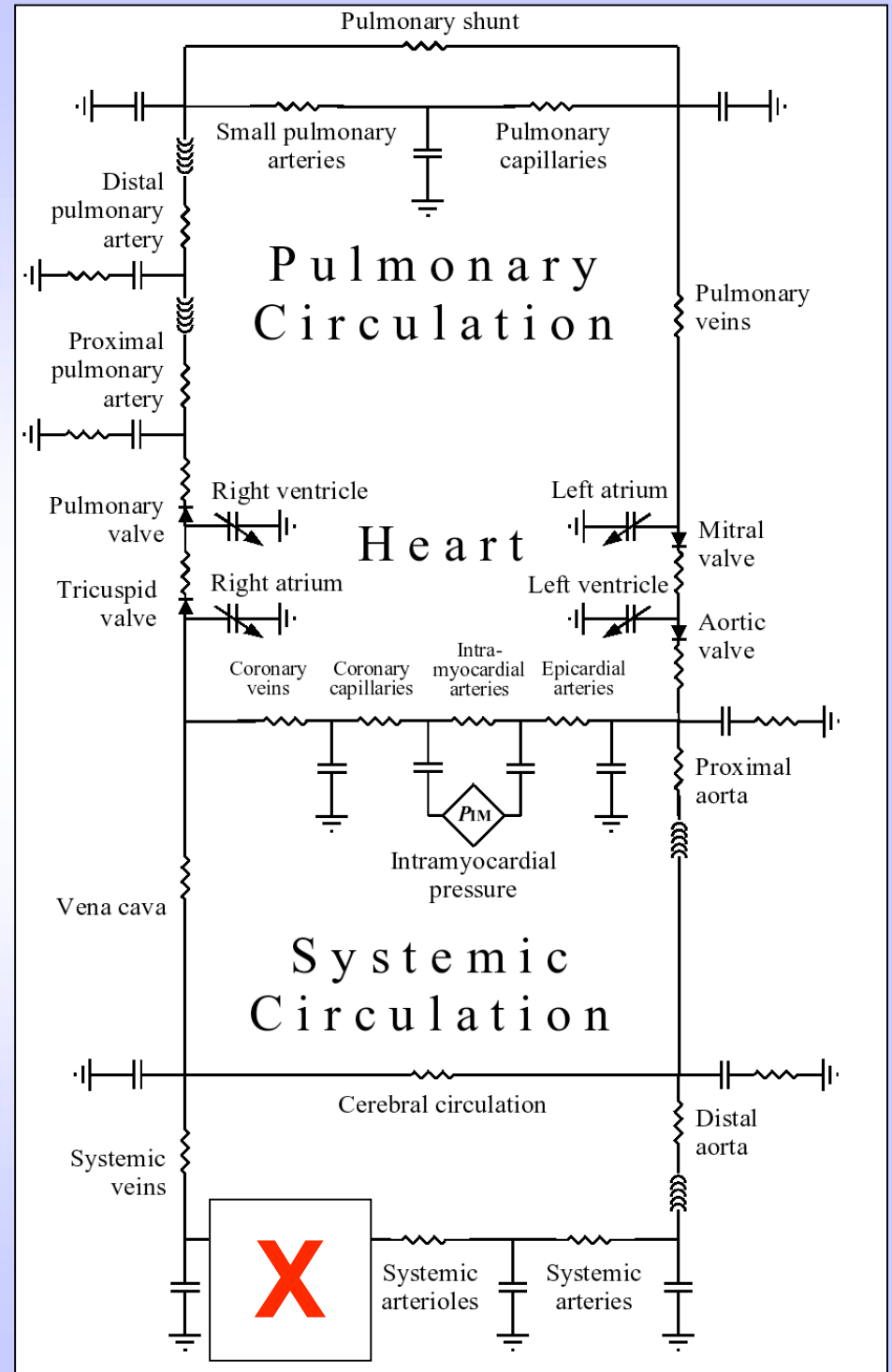Use Poiseuille's Law and the Law of parallel resistors to estimate the number of capillaries in this segment.




Poiseuille's Law relates fluid resistance to vessel length, vessel radius, and fluid viscosity.

$$\Delta P = 8 * \text{Len}_e * \text{Visc} * F / \pi * r^4$$


or
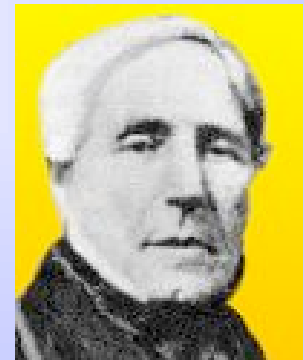
$$R = 8 * \text{Len}_e * \text{Visc} / \pi * r^4$$



The law of parallel resistors
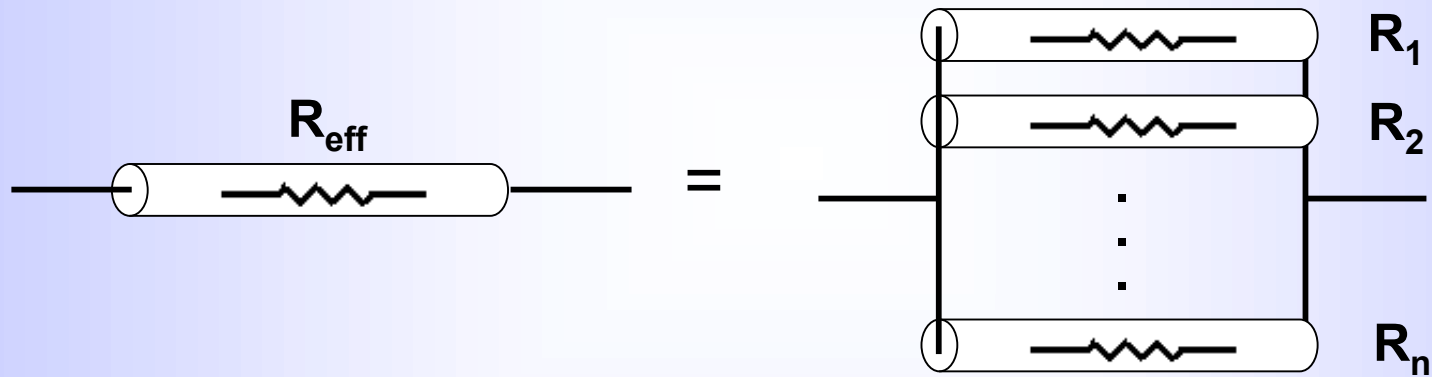
$$1/R_{\text{eff}} = 1/R_1 + 1/R_2 \dots + 1/R_n$$



If all n parallel resistances are equal

$$R_{\text{eff}} = R_1/n$$

Use a 3-element Windkessel capillary segment in *spheart_1.proj* to estimate the number of capillaries in the human peripheral circulation

Declare time-dependent variables (use these codewords):

- Radius of one capillary (um): **rcap**
- Volume of all peripheral capillaries (ml): **Vsc**
- Lumped resistance of capillary segment (mmHg*sec/ml): **Rsc**
- Internal pressure for capillaries (mmHg): **Psc**
- Blood flow through capillaries (ml/sec): **Fsc**

Declare constant parameters (your own codewords):

- Blood viscosity (cp): **5**
- Capillary length (cm): **0.286**
- Initial systemic capillaries volume: **256** (requires a *when(t=t.min) { }* statement)
- Lumped capillary compliance (ml/mmHg): **7.98**
- Total number of capillaries: ???

ASSIGNMENT: Use the equations on the right to solve the variables listed above. Get the model to compile and run. Adjust the number of capillaries until Psc stabilizes around 32 mmHg in the steady state.

Assumptions:

- All capillaries are in parallel
- All capillaries have the same geometry
- All capillaries are cylindrical
- Pressure external to the capillaries is zero
- Unstressed capillary volume is zero

Ohm's Law for fluids

$$F_{out} = \Delta P / R$$

Law of compliance

$$P_{int} - P_{ext} = (V - V_{rest}) / C$$

Kirchoff's Conservation Law

$$dV/dt = F_{in} - F_{out}$$

Poiseuille's Law of resistance

$$R = 8 * Len * Visc / \pi * r^4$$

Volume of one cylinder

$$V = Len * \pi * r^2$$

Law of identical resistors in parallel

$$R_{eff} = R_1 / n$$

****Super awesome extra bonus points for using the JSim optimizer to estimate the number of capillaries!****